EE 363M Spring 2000, Homework Set 2 Wed. Feb. 16; Due: Wed. Feb 23

1. (15 pts) (from: Ramo, problems 5.7b, 5.7g, and 5.7h): Using the general input impedance formula for and L-C T-line:

$$Z_{i} = Z(z = -l) = Z_{o} \frac{Z_{L} + jZ_{o} \tan(\beta l)}{Z_{o} + jZ_{L} \tan(\beta l)}$$

find Z_i when:

- (a) the load is a short.
- (b) the load is an open.
- (c) the line is a half wavelength long line terminated by Z_{L} .
- (d) the line is a quarter wavelength long line terminated by ${
 m Z}_{
 m L}$.
- (e) the line length is <u>not</u> near a quarter wavelength and $Z_L << Z_o$.

hint: use the first order terms of a binomial expansion for Z_i to show that $Z_i = i \frac{1}{2} \tan(\theta_i) + \frac{1}{2} \tan^2(\theta_i)$

$$Z_i \approx j Z_o \tan(\beta l) + Z_L \sec^2(\beta l)$$

(e) the line length is <u>not</u> near a quarter wavelength and $Z_L >> Z_0$.

hint: use the first order terms of a binomial expansion for $\, Z_i \,$ to show that

$$Z_{i} \approx -jZ_{o} \cot(\beta l) + \frac{Z_{o}^{2}}{Z_{L}} \csc^{2}(\beta l)$$

2. (10 pts) Consider a "general" RLGC transmission line as shown below:



Recall that the input impedance for a generalized T-line is:

$$Z_{i} = Z(z = -l) = Z_{o} \frac{Z_{L} + Z_{o} \tanh(\gamma l)}{Z_{o} + Z_{L} \tanh(\gamma l)}$$

Plot the "effective" capacitance versus frequency (use a log frequency scale, and go from "low" frequency up to 10 GHz) for a 10 cm long line with a 10 pF load, where $C_{\rm effective}$ is given by:

$$C_{\text{effective}} = \frac{-1}{\omega \cdot Im(Z_i)}$$

On the same plot, plot the effective capacitance obtained using the two circuit models shown below:



Any comments??